

CS-150

Coursework-3

i) False, Binary 1 is usually in the range of 2v-5v

ii) False, for they give the same output when both inputs are the same

→ NAND

A	B	X
0	0	1
1	1	0

NOR

A	B	X
0	0	1
1	1	0

iii) True

iv) True -  $(A+B)' = A'B'$

v) False XOR →

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

vi) True

b)i) An incoming voltage of ~~0.8v~~ 0.8v or below (anything above zero) is read as low(0) and a voltage between 2v-5v is read as High (1)


ii) A gate consists of one component (the gate ~~itself~~ itself) while circuits are made up of multiple gates

iii) Boolean expressions  
Truth Tables  
Circuit diagrams

c)

	A	B	C	X
i)	0	0	0	1
	0	0	1	0
	0	1	0	1
	0	1	1	0
	1	0	0	1
	1	0	1	0
	1	1	0	0
	1	1	1	1

ii)  $X = (A \cdot B)' + (C \cdot D)'$

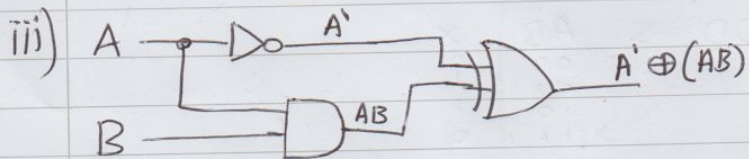

iv)

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1